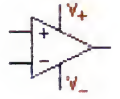


## OPERATIONAL AMPLIFIERS



The Operational Amplifier has two voltage supplies  $+V$  and  $-V$  which are usually omitted from schematics. The other two inputs marked with a  $-$  and a  $+$  are called the inverting input and the non-inverting input respectively. How these inputs are used determines what the output signal will be.

See [Field Effect Transistors](#) for information on the theory for the construction of the Op Amp.


<i>Ideal Operational Amplifier</i>	<i>Real Operational Amplifier</i>
$\text{Gain} = \infty$ $R_{in}$ very high $R_{out} = 0$ $v_- = v_+$ $I_{in} = 0$	$\text{Gain} \sim 80 \text{ to } 100 \text{ dB}$ $R_{in} \sim 10^{10} \text{ to } 10^{12}$ $R_{out}$ is small $\sim 10 \Omega$ $V_{out} = A_v (v_+ - v_-)$ $v_+ - v_-$ is small $I_{in}$ is very small $\sim 10^{-12} \text{ A}$

This table can be used for linear applications of operational amplifiers only. In non-linear applications  $v_{out} \neq A_v (v_+ - v_-)$

### Inverting Amplifiers


When the input goes more positive, the output goes more negative (and vice versa).

$$\text{Gain} = -R_2 / R_1$$

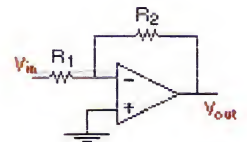


### Noninverting Amplifiers

$$\text{Gain} = 1 + R_2 / R_1$$

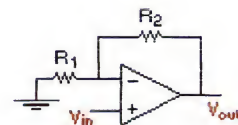
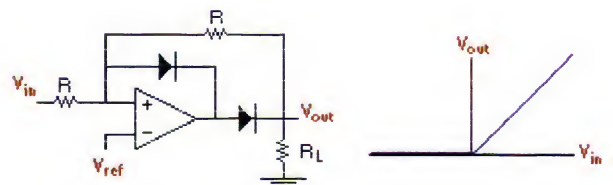
### Perfect Diode

The perfect diode overcomes the imperfection of the diode, by rectifying very small voltages without clipping.




Diodes may be switched for the opposite effect (mirrored about the  $V_{out}$  axis). When  $V_{ref} = 0$  is shown,  $V_{ref}$  may be changed to offset the corner point on  $V_{in}$  axis.

## Low Pass Filters

Butterworth	Bessel	Chebyshev
<i>maximally flat</i> prevents aliasing good for data acquisition all points pass through -3 dB	<i>linear phase</i> time delay	<i>sharp cut-off</i> high selectivity non-linear phase response
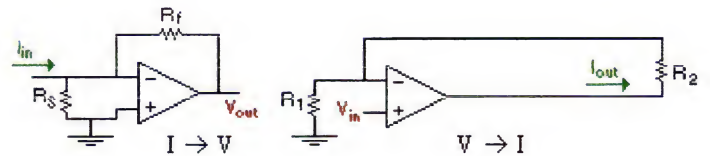
## Transconductance Amplifier

**I to V** is like an ideal amplifier. **V to I** allows a voltage to be measured from a long distance away.




## Threshold Detector

Tend to have +ve feedback, and cannot be analysed using linear equations.

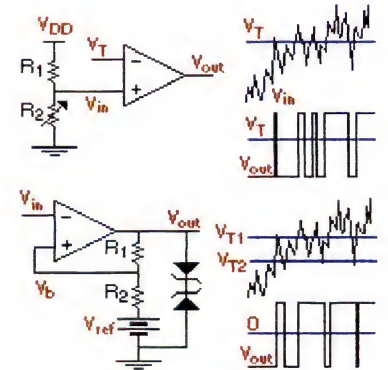example

$$V_{T1} = V_{b1} = \left[ \frac{R_2}{R_1 + R_2} \right] (V_{\text{zener}} - V_{\text{ref}}) + V_{\text{ref}}$$

$$V_{T2} = V_{b2} = \left[ \frac{R_2}{R_1 + R_2} \right] (-V_{\text{zener}} - V_{\text{ref}}) + V_{\text{ref}}$$



## Sensitivity

Sensitivity is how the circuit characteristic changes depending on an the op-amps' characteristic (finite gain) For the basic op-amp circuit shown, The gain of the op-amp is given by  $A_v$ , while the gain of the circuit is given by  $K_v$ .

$$A_v = -R_2 / R_1 \text{ (ideal only)}$$

$$A_v = V_{\text{out}} / (V_+ - V_-) \text{ (non ideal)}$$

$$K_v = \left[ -R_2 / R_1 \right] / \left[ 1 + (1 / A_v) (1 + R_2 / R_1) \right]$$

$$\text{sensitivity} = \Delta K_v / \Delta A_v \text{ (absolute)}$$

$$\text{sensitivity} = (\Delta K_v / K_v) / (\Delta A_v / A_v) \text{ (relative)}$$

